

# INDEX

<b>S. no.</b>	<b>Title</b>	<b>Date</b>
1	Installation of PSpice	
2	Basic gates with C	
3	Half Adder and Full Adder Circuits	
4	Binary Adder-Subtractor Circuit	
5	4-bit Arithmetic Circuit	
6	Circular Shift + Basic logic Circuit	
7	Arithmetic and Logical Unit	
8	3-bit Ripple Counter	
9	BCD to XS-3 and XS-3 to BCD convertor	